

**Precedence** from highest to lowest: Not (!) And (·) Or (+)  
 minterm - product term - SOP - find 1  
 maxterm - sum term - POS - find 0

**Each minterm is the complement of the maxterm**

SOP - 2-level AND-OR/NAND circuit

POS - 2-level OR-AND/NOR circuit

PLAs may not be able to implement a given mapping due to not having enough minterms.

Half Adder:

$$C = X \cdot Y, S = X' \cdot Y + X \cdot Y' = X \oplus Y$$


K-Maps -> SOP

Gate-Level (SSI) Design: Full-Adder, Code Converter

$$C = X \cdot Y + (X \oplus Y) \cdot Z, S = X \oplus (Y \oplus Z)$$


Block-Level Design: block: 4-bit parallel/ripple-carry
 
$$\text{adder: } C_{i+1} = X_i \cdot Y_i + (X_i \oplus Y_i) \cdot C_i, S_i = X_i \oplus Y_i \oplus C_i$$



$$\begin{aligned} X+X \cdot Y &= X & X \cdot Y + X \cdot Z + Y \cdot Z &= X \cdot Y + X' \cdot Z & Y' \cdot Z + Y \cdot Z' &= Y \oplus Z \\ X+X' \cdot Y &= X+Y & Y' \cdot Z' + Y \cdot Z &= (Y \oplus Z)' & X+Y &= (X \oplus Y) + X \cdot Y \end{aligned}$$

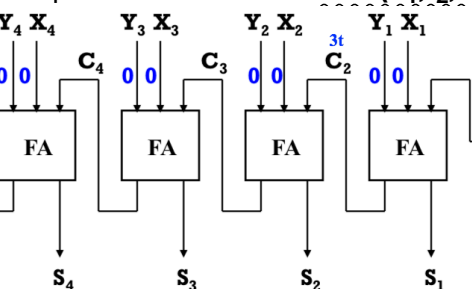
Given a logic gate with delay  $t$ . If inputs are stable at times  $t_1, t_2, \dots, t_n$ , then the earliest time in which the output will be stable is:  $\max(t_1, t_2, \dots, t_n) + t$



Sequential Circuit Design:


S-R Latch:  $Q(t+1) = S + R' \cdot Q, S \cdot R = 0$

Active-High

 

| S | R | $Q(t+1)$      | Comments  |
|---|---|---------------|-----------|
| 0 | 0 | $Q(t)$        | No change |
| 0 | 1 | 0             | Reset     |
| 1 | 0 | 1             | Set       |
| 1 | 1 | indeterminate |           |

Active-Low

 

Gated D Latch:  $Q(t+1) = D$

| EN | D | $Q(t+1)$ | Comments  |
|----|---|----------|-----------|
| 1  | 0 | 0        | Reset     |
| 1  | 1 | 1        | Set       |
| 0  | X | $Q(t)$   | No change |

**combinational circuit:** each output depends entirely on the immediate (present) inputs

**sequential circuit:** each output depends on both present inputs and state

- **Synchronous:** outputs change only at specific time
- **Asynchronous:** outputs change at any time

**Multivibrator:** a class of sequential circuits

§ Bistable (2 stable states)

- Latches and flip-flops.

- differ in the methods used for changing state.

§ Monostable or one-shot (1 stable state)

§ Astable (no stable state)

**Memory element:** a device which can remember value indefinitely, or change value on command from its inputs.

Two types of triggering/activation

- Level/Pulse-triggered

§ Latches

§ ON = 1, OFF = 0


- Edge-triggered

§ Flip-flops

Positive edge-triggered (ON = 0 to 1; OFF = other time)

Negative edge-triggered (ON = 1 to 0; OFF = other time)

input/output = x/y

 

| Present State<br>AB | Next State  |            | Output   |          |
|---------------------|-------------|------------|----------|----------|
|                     | x=0<br>A'B' | x=1<br>A'B | x=0<br>y | x=1<br>y |
| 00                  | 00          | 01         | 0        | 0        |
| 01                  | 00          | 11         | 1        | 0        |
| 10                  | 00          | 10         | 1        | 0        |
| 11                  | 00          | 10         | 1        | 0        |

S-R flip-flop: On the triggering edge of the clock pulse  
 positive edge-triggered S-R flip-flop

T flip-flop: Single input version of the J-K flip-flop  $Q(t+1) = T \cdot Q' + T' \cdot Q$

| T | CLK | $Q(t+1)$ | Comments  |
|---|-----|----------|-----------|
| 0 | ↑   | $Q(t)$   | No change |
| 1 | ↑   | $Q(t)'$  | Toggle    |

| S | R | CLK | $Q(t+1)$ | Comments  |
|---|---|-----|----------|-----------|
| 0 | 0 | X   | $Q(t)$   | No change |
| 0 | 1 | ↑   | 0        | Reset     |
| 1 | 0 | ↑   | 1        | Set       |
| 1 | 1 | ↑   | ?        | Invalid   |

**X = irrelevant ("don't care")**


↑ = clock transition LOW to HIGH

D flip-flop: On the triggering edge of the clock pulse


| D | CLK | $Q(t+1)$ | Comments |
|---|-----|----------|----------|
| 1 | ↑   | 1        | Set      |
| 0 | ↑   | 0        | Reset    |

↑ = clock transition LOW to HIGH

 J-K flip-flop: Q and Q' are fed back to the pulse-steering NAND gates.



 A positive edge-triggered D flip-flop formed with an S-R flip-flop.



| J | K | CLK | $Q(t+1)$ | Comments  |
|---|---|-----|----------|-----------|
| 0 | 0 | ↑   | $Q(t)$   | No change |
| 0 | 1 | ↑   | 0        | Reset     |
| 1 | 0 | ↑   | 1        | Set       |
| 1 | 1 | ↑   | $Q(t)'$  | Toggle    |



**decoder:** Convert binary information from  $n$  input lines to (a maximum of)  $2^n$  output lines.

- Known as  $n$ -to- $m$ -line decoder, or simply  $n:m$  or  $n \times m$  decoder ( $m \leq 2^n$ ).
- May be used to generate  $2^n$  minterms of  $n$  input variables.

SOP = decoder to generate minterms + OR gate to form the sum


**enable control signal:** the device is only activated when the enable  $E = 1$  (one-enable) (MSI is mainly 0-enable)

| X | Y | F <sub>0</sub> | F <sub>1</sub> | F <sub>2</sub> | F <sub>3</sub> |
|---|---|----------------|----------------|----------------|----------------|
| 0 | 0 | 1              | 0              | 0              | 0              |
| 0 | 1 | 0              | 1              | 0              | 0              |
| 1 | 0 | 0              | 0              | 1              | 0              |
| 1 | 1 | 0              | 0              | 0              | 1              |

  

**encoder:** exactly one input line is high and the rest are low,

$$D_0 = F_1 + F_3, D_1 = F_2 + F_3$$

 

| F <sub>0</sub> | F <sub>1</sub> | F <sub>2</sub> | F <sub>3</sub> | D <sub>1</sub> | D <sub>0</sub> |
|----------------|----------------|----------------|----------------|----------------|----------------|
| 1              | 0              | 0              | 0              | 0              | 0              |
| 0              | 1              | 0              | 0              | 0              | 1              |
| 0              | 0              | 1              | 0              | 1              | 0              |
| 0              | 0              | 0              | 1              | 1              | 1              |
| 0              | 0              | 0              | 0              | X              | X              |
| 0              | 1              | 0              | 1              | X              | X              |
| 0              | 1              | 1              | 0              | X              | X              |
| 0              | 1              | 1              | 1              | X              | X              |
| 1              | 0              | 0              | 1              | X              | X              |
| 1              | 0              | 1              | 0              | X              | X              |
| 1              | 0              | 1              | 1              | X              | X              |
| 1              | 1              | 0              | 0              | X              | X              |
| 1              | 1              | 0              | 1              | X              | X              |
| 1              | 1              | 1              | 0              | X              | X              |
| 1              | 1              | 1              | 1              | X              | X              |

**multiplexer:** It steers one of  $2^n$  inputs to a single output line, using  $n$  selection lines. Also known as a **data selector**.



- A number of input lines
- A number of selection lines
- One output line
- Output of multiplexer is "sum of the (product of *data lines* and *selection lines*)"

Example: Output of a 4-to-1 multiplexer is:  $Y =$


$$I_0 \cdot (S_1' \cdot S_0') + I_1 \cdot (S_1' \cdot S_0) + I_2 \cdot (S_1 \cdot S_0') + I_3 \cdot (S_1 \cdot S_0) = I_0 \cdot m_0 + I_1 \cdot m_1 + I_2 \cdot m_2 + I_3 \cdot m_3$$

| I <sub>0</sub> | I <sub>1</sub> | I <sub>2</sub> | I <sub>3</sub> | S <sub>1</sub> | S <sub>0</sub> | Y              |
|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| d <sub>0</sub> | d <sub>1</sub> | d <sub>2</sub> | d <sub>3</sub> | 0              | 0              | d <sub>0</sub> |
| d <sub>0</sub> | d <sub>1</sub> | d <sub>2</sub> | d <sub>3</sub> | 0              | 1              | d <sub>1</sub> |
| d <sub>0</sub> | d <sub>1</sub> | d <sub>2</sub> | d <sub>3</sub> | 1              | 0              | d <sub>2</sub> |
| d <sub>0</sub> | d <sub>1</sub> | d <sub>2</sub> | d <sub>3</sub> | 1              | 1              | d <sub>3</sub> |


| S <sub>1</sub> | S <sub>0</sub> | Y              |
|----------------|----------------|----------------|
| 0              | 0              | I <sub>0</sub> |
| 0              | 1              | I <sub>1</sub> |
| 1              | 0              | I <sub>2</sub> |
| 1              | 1              | I <sub>3</sub> |

  

 A  $2^n$ -to-1-line multiplexer, or simply  $2^n:1$  MUX, is made from an  $n:2^n$  decoder by adding to it  $2^n$  input lines, one to each AND gate.



© #18: MSI Components

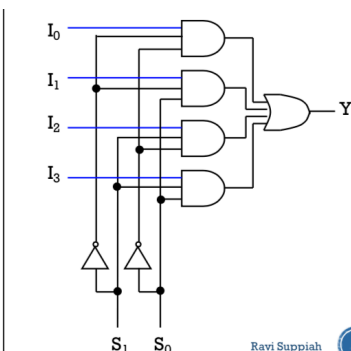

Ravi Suppiah


**priority encoder:**

- If two or more inputs are equal to 1, the input with the highest priority takes precedence.
- If all inputs are 0, this input combination is considered invalid.

| Inputs         |                |                |                | Outputs |   |   |
|----------------|----------------|----------------|----------------|---------|---|---|
| D <sub>0</sub> | D <sub>1</sub> | D <sub>2</sub> | D <sub>3</sub> | f       | g | V |
| 0              | 0              | 0              | 0              | X       | X | 0 |
| 1              | 0              | 0              | 0              | 0       | 0 | 1 |
| X              | 1              | 0              | 0              | 0       | 1 | 1 |
| X              | X              | 1              | 0              | 1       | 0 | 1 |
| X              | X              | X              | 1              | 1       | 1 | 1 |

**demultiplexers:** Given an input line and a set of selection lines, a **demultiplexer** directs data from the input to one selected output line.

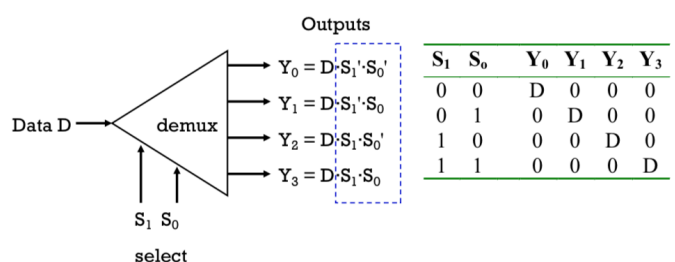demultiplexer circuit is actually identical to a decoder with enable.



| Q | Q <sup>+</sup> | J | K |
|---|----------------|---|---|
| 0 | 0              | 0 | X |
| 0 | 1              | 1 | X |
| 1 | 0              | X | 1 |
| 1 | 1              | X | 0 |

**J/K Flip-flop**

| Q | Q <sup>+</sup> | S | R |
|---|----------------|---|---|
| 0 | 0              | 0 | X |
| 0 | 1              | 1 | 0 |
| 1 | 0              | 0 | 1 |
| 1 | 1              | X | 0 |


**SR Flip-flop**

| Q | Q <sup>+</sup> | D |
|---|----------------|---|
| 0 | 0              | 0 |
| 0 | 1              | 1 |
| 1 | 0              | 0 |
| 1 | 1              | 1 |

**D Flip-flop**

| Q | Q <sup>+</sup> | T |
|---|----------------|---|
| 0 | 0              | 0 |
| 0 | 1              | 1 |
| 1 | 0              | 1 |
| 1 | 1              | 0 |

**T Flip-flop**

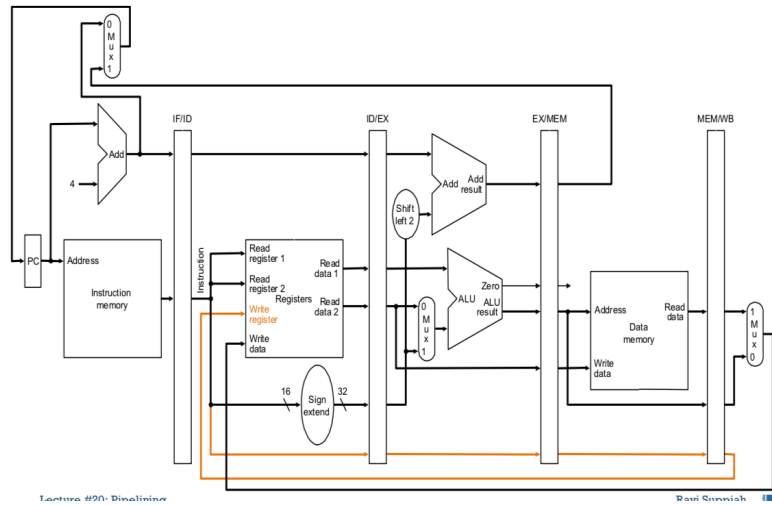

- § **IF**: Instruction Fetch
- § **ID**: Instruction Decode and Register Read
- § **EX**: Execute an operation or calculate an address
- § **MEM**: Access an operand in data memory
- § **WB**: Write back the result into a register
- At the end of a cycle, **IF/ID** receives (stores):
  - Instruction read from InstructionMemory[ PC ]
  - PC + 4
- PC + 4
  - Also connected to one of the MUX's inputs (another coming later)

| At the beginning of a cycle<br><b>IF/ID</b> register supplies:  | At the end of a cycle<br><b>ID/EX</b> receives:           |
|-----------------------------------------------------------------|-----------------------------------------------------------|
| ❖ Register numbers for reading two registers                    | ❖ Data values read from register file                     |
| ❖ 16-bit offset to be sign-extended to 32-bit                   | ❖ 32-bit immediate value                                  |
| ❖ PC + 4                                                        | ❖ PC + 4                                                  |
| At the beginning of a cycle<br><b>ID/EX</b> register supplies:  | At the end of a cycle<br><b>EX/MEM</b> receives:          |
| ❖ Data values read from register file                           | ❖ (PC + 4) + (Immediate x 4)                              |
| ❖ 32-bit immediate value                                        | ❖ ALU result                                              |
| ❖ PC + 4                                                        | ❖ isZero? signal                                          |
|                                                                 | ❖ Data Read 2 from register file                          |
| At the beginning of a cycle<br><b>EX/MEM</b> register supplies: | At the end of a cycle<br><b>MEM/WB</b> receives:          |
| ❖ (PC + 4) + (Immediate x 4)                                    | ❖ ALU result                                              |
| ❖ ALU result                                                    | ❖ Memory read data                                        |
| ❖ isZero? signal                                                |                                                           |
| ❖ Data Read 2 from register file                                |                                                           |
| At the beginning of a cycle<br><b>MEM/WB</b> register supplies: | At the end of a cycle                                     |
| ❖ ALU result                                                    | ❖ Result is written back to register file (if applicable) |
| ❖ Memory read data                                              | ❖ <b>There is a bug here.....</b>                         |

|        | EX Stage |        |       |     | MEM Stage |           |        | WB Stage  |           |
|--------|----------|--------|-------|-----|-----------|-----------|--------|-----------|-----------|
|        | RegDst   | ALUSrc | ALUOp |     | Mem Read  | Mem Write | Branch | MemTo Reg | Reg Write |
|        |          |        | op1   | op0 |           |           |        |           |           |
| R-type | 1        | 0      | 1     | 0   | 0         | 0         | 0      | 0         | 1         |
| lw     | 0        | 1      | 0     | 0   | 1         | 0         | 0      | 1         | 1         |
| sw     | X        | 1      | 0     | 0   | 0         | 1         | 0      | X         | 0         |
| beq    | X        | 0      | 0     | 1   | 0         | 0         | 1      | X         | 0         |


Single Cycle  
 § Cycle time:  
 §  $CT_{seq} = \sum_{k=1}^N T_k$   
 §  $T_k$  = Time for operation in stage k  
 § N = Number of stages  
 § Total Execution Time for **I** instructions:

Multi Cycle  
 § Cycle time:  
 §  $CT_{multi} = \max(T_k)$   
 §  $\max(T_k)$  = longest stage duration among the N stages  
 § Total Execution Time for **I** instructions:  
 §  $Time_{multi} = Cycles \times CycleTime = I \times Average$


$CPI \times CT_{multi}$   
 § **Average** CPI is needed because each instruction takes different number of cycles to finish

Pipeline Cycle  
 § Cycle time:  
 §  $CT_{pipeline} = \max(T_k) + T_d$   
 §  $\max(T_k)$  = longest time among the N stages  
 §  $T_d$  = Overhead for pipelining, e.g. pipeline register  
 § Cycles needed for **I** instructions:  
 §  $I + N - 1$   
 § **N - 1** is the cycles wasted in filling up the pipeline  
 § Total Execution Time for **I** instructions:  
 §  $Time_{pipeline} = Cycle \times CT_{pipeline} = (I + N - 1) \times (\max(T_k) + T_d)$


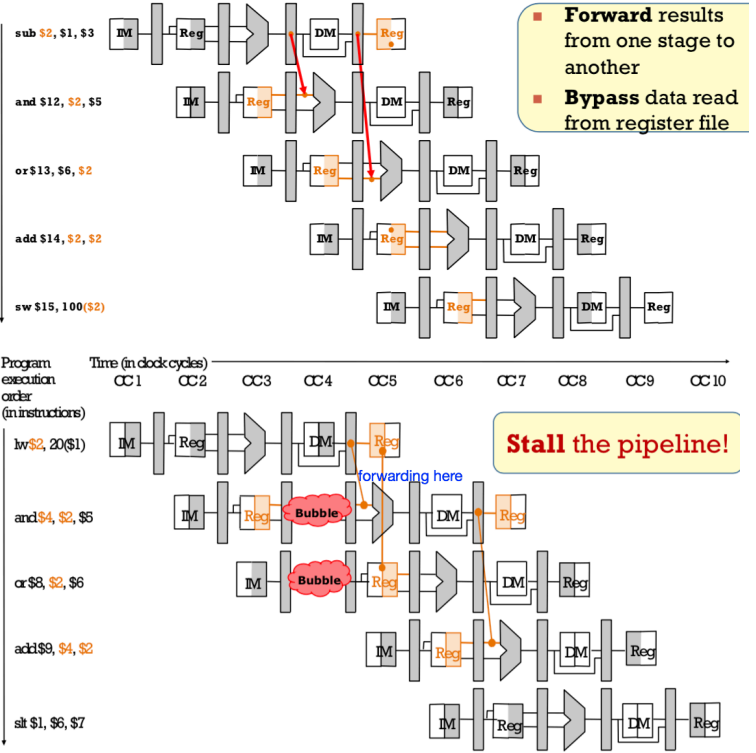
Ideal Speedup  
 • Every stage takes the same amount of time  
 • No pipeline overhead  $T_d=0$   
 • Number of instructions I is much larger than number of stages N  
 $Speedup_{pipeline} = Time_{seq} / Time_{pipeline}$   
 Pipeline processor can gain **N** times speedup, where **N** is the number of pipeline stages



## 6.1 REDUCE STALLS: EARLY BRANCH (3/3)

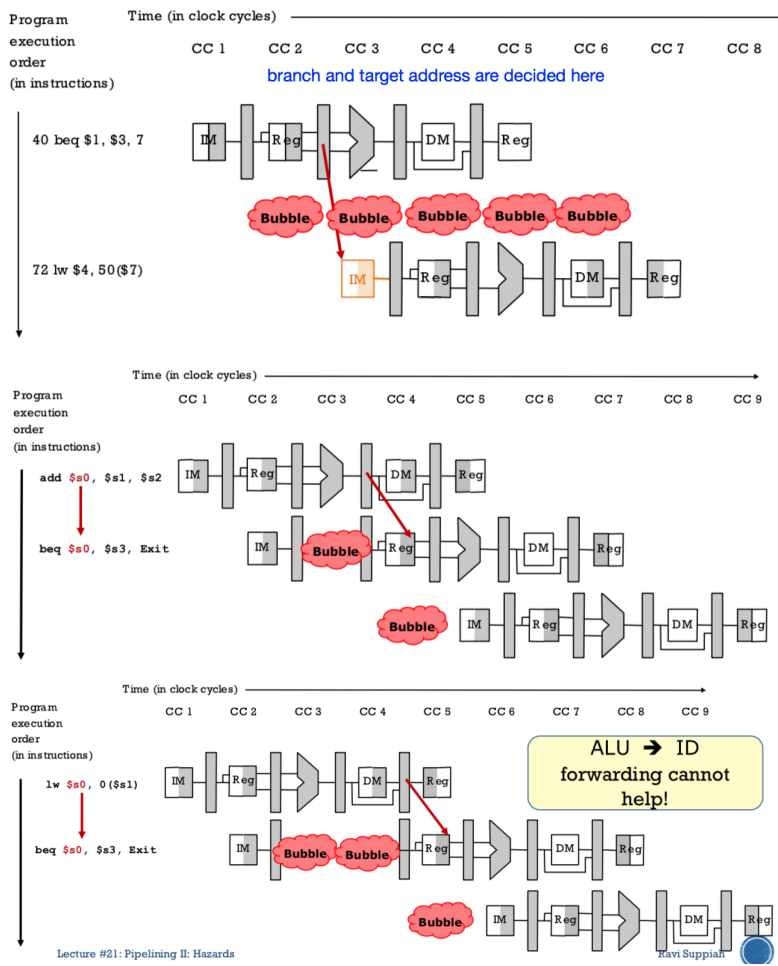

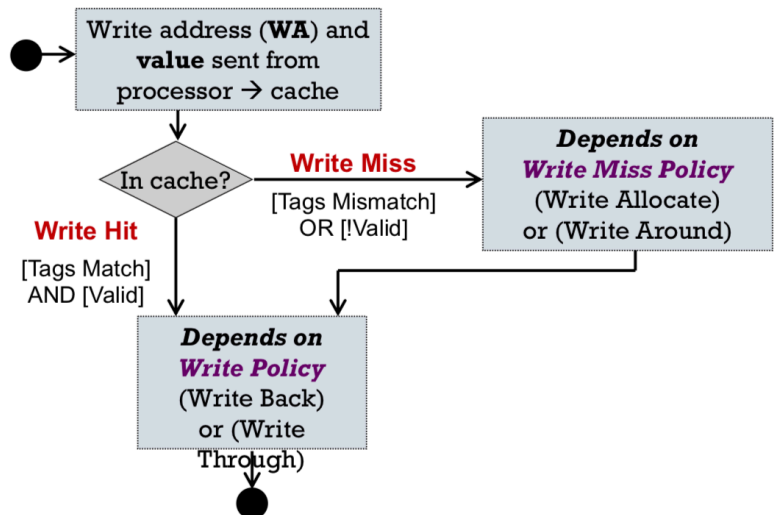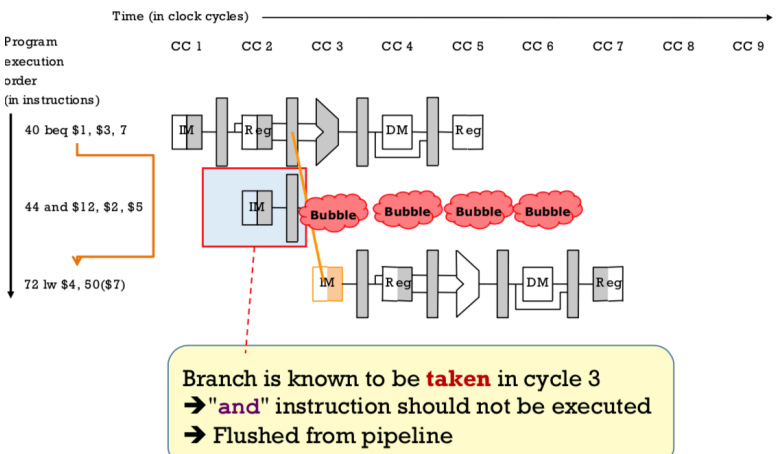
## 6.2 BRANCH PREDICTION: WRONG PREDICTION





- Hit:** Data is in cache (e.g., X)
  - Hit rate:** Fraction of memory accesses that hit
  - Hit time:** Time to access cache
  - Miss:** Data is not in cache (e.g., Y)
  - Miss rate** = 1 – Hit rate
  - Miss penalty:** Time to replace cache block + hit time
  - Hit time < Miss penalty
- Average Access Time = Hit rate x Hit Time + (1-Hit rate) x Miss penalty

## 3. MEMORY TO CACHE MAPPING (2/2)

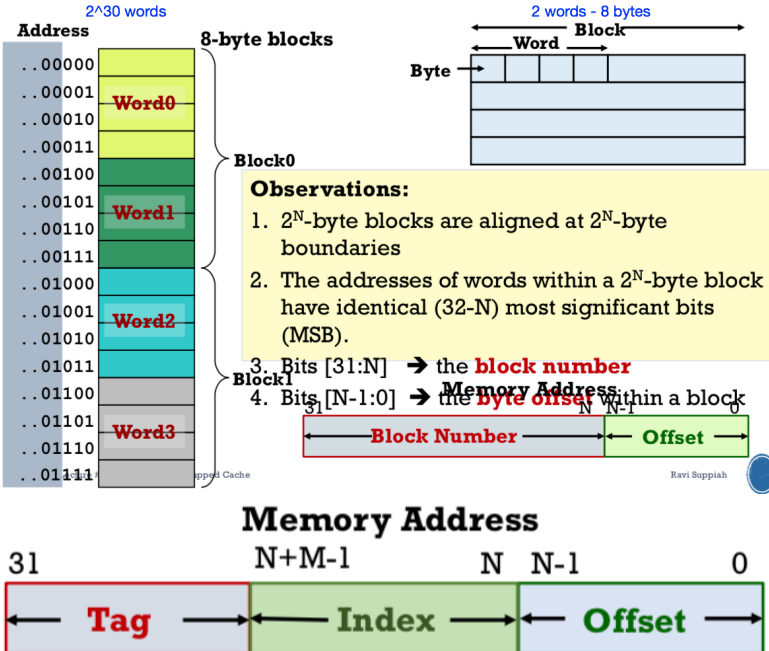

Cache Block size = 2<sup>N</sup> bytes

Number of cache blocks = 2<sup>M</sup>

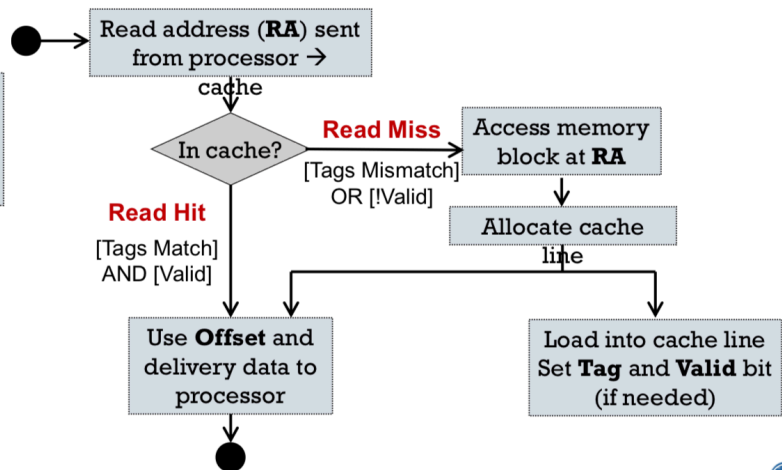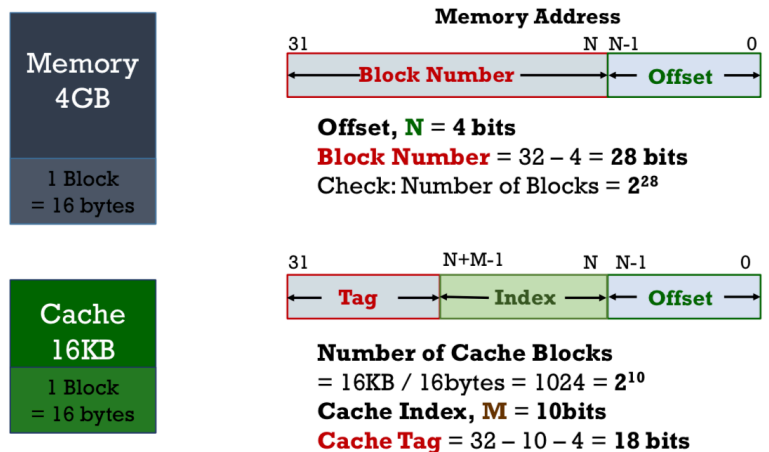




7PIs, 4EPIs

How mar  
How mar


| CD | AB |    |    |    |
|----|----|----|----|----|
|    | 00 | 01 | 11 | 10 |
| 00 | 1  | 1  | 0  | 1  |
| 01 | 0  | 0  | 1  | 1  |
| 11 | 1  | 1  | 0  | 1  |
| 10 | 1  | 0  | 1  | 1  |

 


- Exercise: What modifications should be made to provide an ENABLE input for the 3×8 decoder and the 4×16 decoder created in the previous two examples?
- Exercise: How to construct a 4×16 decoder using five 2×4 decoders with enable?
 
## 2. DECODERS: IMPLEMENTING FUNCTIONS REVISIT (2/2)


$$f(Q,X,P) = \sum m(0,1,4,6,7) = \prod M(2,3,5)$$




(a) Active-high decoder with OR gate.

 

(b) Active-low decoder with NAND gate.

 

(c) Active-high decoder with NOR gate.

 

(d) Active-low decoder with AND gate.

### Write operation:

- Transfers the address of the desired word to the address lines.
- Transfers the data bits (the word) to be stored in memory to the data input lines.
- Activates the Write control line (set Read/Write to 0).

### Read operation:

- Transfers the address of the desired word to the address lines.
- Activates the Read control line (set Read/Write to 1).

| Memory Enable | Read/Write | Memory Operation        |
|---------------|------------|-------------------------|
| 0             | X          | None                    |
| 1             | 0          | Write to selected word  |
| 1             | 1          | Read from selected word |

- Two types of RAM
- Static RAMs use flip-flops as the memory cells.
- Dynamic RAMs use capacitor charges to represent data. Though simpler in circuitry, they have to be constantly refreshed.